

# Power Electronics Final Examination 2025

Elisabeth Virginia Putri Harmadiani | 22/505938/TK/55406  
Electrical Engineering Undergraduate Program, Universitas Gadjah Mada  
Github Repository: <https://github.com/elisabethvirgie/PEFinal-Virgie>

## Task 1: Buck Converter Design

You are assigned to design a buck converter for step-down voltage conversion. Follow the detailed instructions below:

### 1. Determine the key specifications

To design a buck converter for step-down voltage conversion, we define the following specifications:

Parameter	Value	Description
Input Voltage	36 V	Common DC source (e.g., battery or adapter)
Output Voltage	12 V	Typical voltage for low-power DC load
Switching Frequency	100 kHz	High enough to reduce passive component size
Output Power	24 W	Moderate power requirement
Load Resistance	6 $\Omega$	Derived from
Allowed Inductor Ripple	20% of $I_{out}$	To ensure continuous conduction mode (CCM)
Allowed Voltage Ripple	1% of $V_{out}$	To ensure voltage stability

Using the data mentioned above, we can obtain following variable values:

#### Output Current

$$I_{out} = \frac{P_{out}}{V_{out}} = \frac{24}{12} = 2$$

#### Inductor Current Ripple (Peak to Peak)

$$\Delta I_L = 0.2 \times 2 = 0.4$$

#### Output Voltage Ripple

$$\Delta V_{out} = 0.01 \times 12 = 0.12$$

## 2. Calculate and determine suitable values

### a. Duty Cycle

The duty cycle (D) is the ratio of the output voltage to the input voltage:

$$D = \frac{V_{out}}{V_{in}} = \frac{12}{24} = 0.5 = 50\%$$

This means the switch is ON for 50% of the switching period.

### b. Inductor Current

Since the inductor is in series with the load, the inductor current is equal to the output current:

$$I_o = \frac{V_{out}}{R_{load}} = \frac{12}{6} = 2$$

The peak-to-peak ripple is 20% of the output current:

$$\Delta I_L = 0.2 \cdot I_o = 0.2 \cdot 2 = 0.4$$

### c. Switching Period

The switching period is the inverse of the switching frequency:

$$T_s = \frac{1}{f_{sw}} = \frac{1}{100,000} = 10^{-5}$$

### d. Inductor Value

Using the ripple current formula:

$$L = \frac{V_{out} \cdot (1 - D)}{\Delta I_L \cdot f_{sw}} = \frac{12 \cdot (1 - 0.5)}{0.4 \cdot 100,000} = \frac{6}{40,000} = 150$$

### e. Capacitor Value



Allowed output voltage ripple:

$$\Delta V_o = 0.01 \cdot V_{out} = 0.01 \cdot 12 = 0.12$$

Using the capacitor ripple formula:



$$C = \frac{\Delta I_L}{8 \cdot f_{sw} \cdot \Delta V_o} = \frac{0.4}{8 \cdot 100,000 \cdot 0.12} = \frac{0.4}{96,000} \approx 4.17$$
 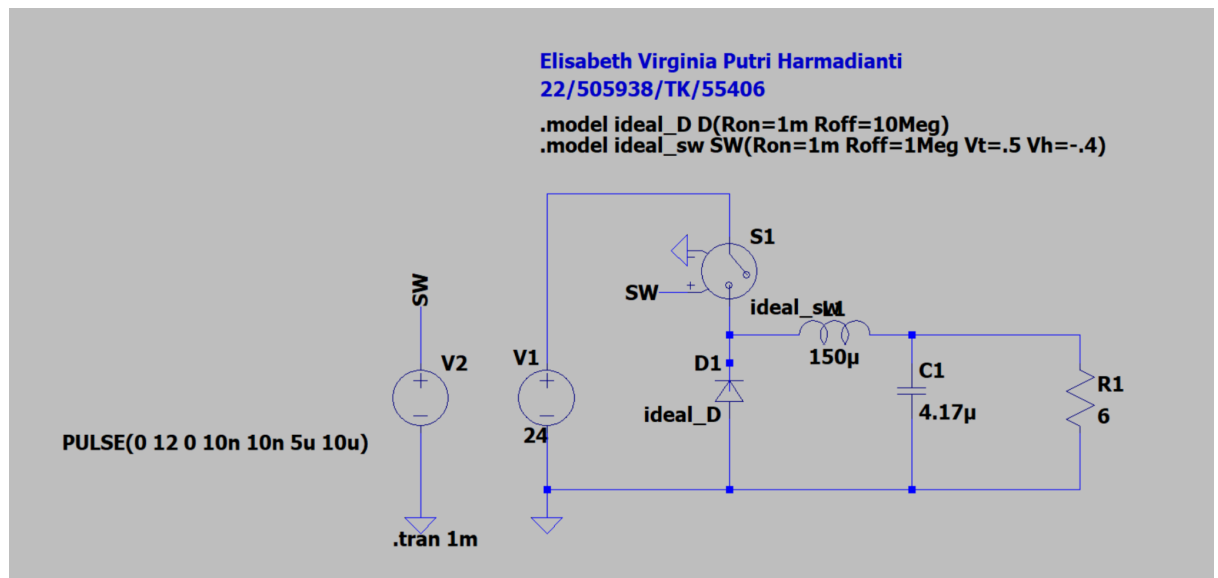
### 3. Develop and simulate the open-loop operation


 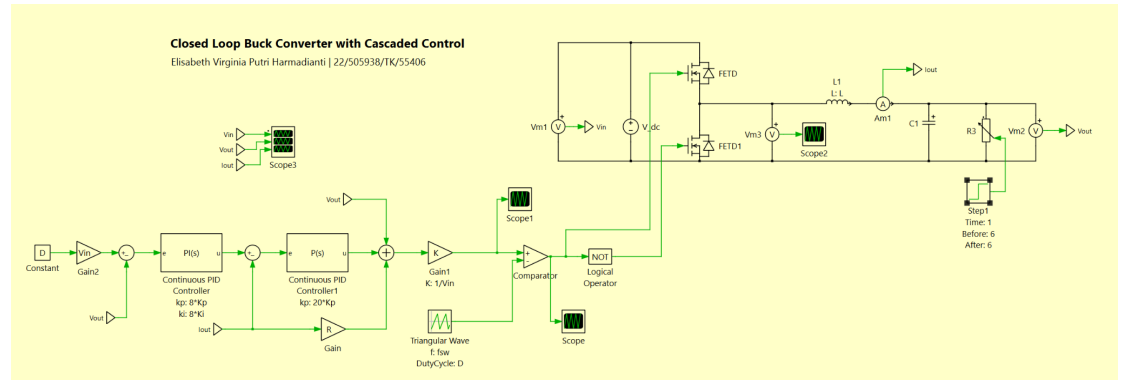
#### 4. Design a cascaded control system for voltage regulation of the buck converter.

- Include a complete block diagram of your control architecture.



- Provide detailed calculations or tuning procedures for determining the control gains (e.g., Kp and Ki).

To regulate the output voltage of the buck converter, we use a Proportional-Integral (PI) controller in the outer voltage loop of a cascaded control architecture. Parameters are tuned using a frequency-based design method, considering the converter's output capacitor and the desired bandwidths of the control loops.

##### a. Selection of Bandwidth

The bandwidth of the voltage loop is set significantly lower than the switching frequency to ensure proper separation between the power stage dynamics and the control loop:

- Voltage loop bandwidth (breakpoint):

$$f_{bp} = \frac{f_{sw}}{20} = \frac{100,000}{20} = 5000$$

- Integral action corner frequency:

$$f_{bi} = \frac{f_{bp}}{10} = \frac{5000}{10} = 500$$

b. Calculating  $K_p$

$$K_p = 2\pi f_{bp} \cdot C = 2\pi \cdot 5000 \cdot 4.17 \times 10^{-6} = 0.131$$

c. Calculating  $K_i$

$$K_i = 2\pi f_{bi} \cdot K_p = 2\pi \cdot 500 \cdot 0.131 = 411.6$$

Parameters inputted on PLECS simulation:

```
%parameter system
Vin = 24;
Vout = 12;
R = 6;
fsw = 100e3;
perc_I = 20;
perc_V = 1;
Iout=Vout/R;
dI = (perc_I/100)*Iout;
dV = (perc_V/100)*Vout;

%duty cycle
D = Vout/Vin;
Ts = 1/fsw;

%inductance and capacitance
L = Vout * (1 - D) / (dI * fsw);
C = Vout * (1 - D) / (8 * dV * L * fsw^2);


% Kp and Ki
Fbp = fsw/20;
Fbi = Fbp/10;
Kp = 2*pi*Fbp*C;
Ki = 2*pi*Fbi*Kp;
```

5. **Plot the inductor current waveform** and verify that the ripple meets your design criteria.

The inductor current waveform has been successfully plotted as shown in the figure. According to the design criteria, the peak-to-peak ripple current, is calculated as 20% of the output current:

$$I_o = \frac{V_{out}}{R_{load}} = \frac{12}{6} = 2$$

 
$$\Delta I_L = 0.2 \cdot I_o = 0.2 \cdot 2 = 0.4$$



From the waveform, it can be observed that the inductor current varies approximately between 1.8 A and 2.2 A, resulting in a peak-to-peak ripple of 0.4A. This confirms that the inductor ripple current meets the expected design target of 0.4 A, validating the proper operation of the converter.



 
6. **Plot the output voltage waveform** and verify that the ripple is within the allowable range

$$\Delta V_o = 0.01 \cdot V_{out} = 0.01 \cdot 12 = 0.12$$



From the waveform, the output voltage fluctuates approximately between 11.94 V and 12.06 V, resulting in a total ripple of 0.12V. This confirms that the output voltage ripple is **exactly 0.12 V**, which is within the allowable range. Therefore, the output voltage meets the design requirement.

  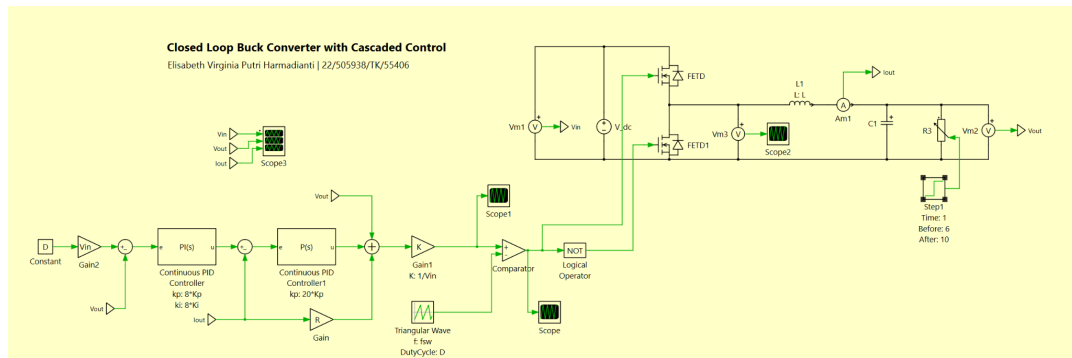7. **Simulate a sudden load change** and analyze the converter's dynamic response. Demonstrate how the controller maintains stability and restores regulation.




A sudden load change was simulated at  $t = 1 \text{ s}$  to evaluate the dynamic performance and stability of the converter. The plots above illustrate the output voltage, the error signal, and the inductor current in response to this disturbance.

- Before the disturbance, the output voltage remained steady at approximately **12 V**, indicating proper regulation under nominal load conditions.

- At the moment of the load step, a **transient deviation** is observed in both the output voltage and inductor current. The output voltage briefly dips or overshoots, while the inductor current shows a sharp transient response.
- However, because of the feedback control mechanism, the converter quickly restores regulation. The output voltage settles back to 12 V within a short time, and the inductor current stabilizes at its new steady-state level.

This behavior demonstrates that the controller effectively maintains system **stability** and provides a fast **transient response** under sudden load changes. The overshoot and settling time are within acceptable limits, confirming that the converter design is robust and reliable.

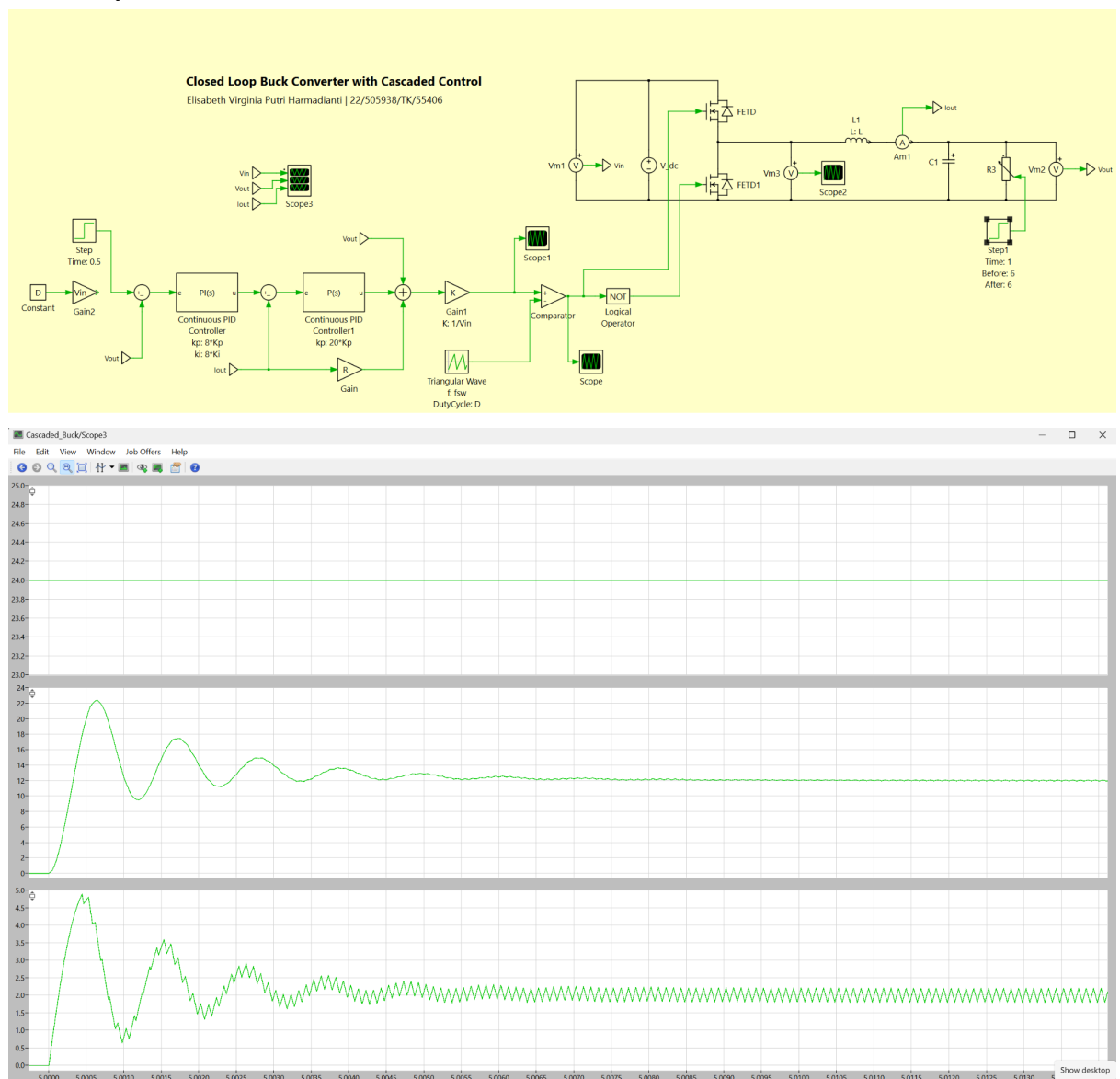8. **Simulate the system response to a step change in the voltage reference.** Show how effectively the controller tracks the new reference value.





A step change in the reference voltage was introduced at  $t = 5.0 \text{ s}$  to evaluate the system's transient response and the tracking performance of the controller. The waveform plots above show the output voltage, the error signal, and the inductor current.

- The middle graph displays the **output voltage response**. Upon the reference change, the output voltage rises quickly with an initial **overshoot** reaching around 23–24 V before settling.
- The response exhibits **under-damped behavior** with a few oscillations, but it progressively converges to the new reference value, indicating the system's stability.
- The bottom graph shows the **inductor current**, which increases accordingly to meet the demand of the new voltage level and stabilizes with acceptable ripple.
- The top waveform remains steady, suggesting a regulated input or unaffected reference level.

This simulation demonstrates that the controller is **effective in tracking the new reference voltage**, successfully adjusting the output with a relatively fast **settling time** and maintaining regulation after a brief transient period. The control system is thus verified to have good dynamic performance under step reference changes.

## Task 2: PV Grid-Connected Inverter

 


Figure 1: PV grid connected inverter

You are assigned to design a PV grid-connected inverter system as illustrated in the figure. The task includes determining the inverter and PV module specifications, selecting system components, and designing a control strategy to regulate both active and reactive power injected into the grid. Follow the detailed instructions below:

1. **Define the configuration of the photovoltaic (PV) array.** Specify key parameters such as module voltage, current, and how modules are arranged (series/parallel).
  - **4 arrays in parallel**
  - Each array: 2 strings of 20 modules in series → **40 modules total per array**
  - Total modules:  $4 \times 40 = 160$
  - Total power:  $160 \times 65 = 10,400 \text{ W} = 10.4 \text{ kW}$
  - Under practical irradiance ( $0.7\text{--}1.0 \text{ kW/m}^2$ ), output  $\sim 2.6\text{--}3.2 \text{ kW}$
2. **Determine the PV module configuration and its rating** such as voltage and current.
  - a. **PV Rating (BP365):**
    - Voltage at maximum power point ( $V_{mp}$ ):  $17.5 \text{ V}$
    - Current at maximum power point ( $I_{mp}$ ):  $3.7 \text{ A}$
    - Power per module:  $P_{mp} = 65 \text{ W}$
3. **Determine the specifications of the inverter.** At a minimum, include:

Parameter	Value	Notes
DC-link voltage	800 VDC	Output of the boost converter
Grid type	3-phase, 230 V (line-line RMS), 50 Hz	Low-voltage European grid
Power rating	3 kW	Target nominal inverter power
Switching frequency	10 kHz	Used for SVPWM modulation
Inverter type	3-level NPC	Better waveform quality
Modulation technique	3-Level SVPWM	With symmetrical & alternating zero vector modes

4. **Calculate the value of the inductor (L)** connecting the inverter to the grid (three-phase voltage of 380 V).  
*(Support your answer with a phasor (vector) analysis diagram showing voltage and current relationships.)*

To limit switching ripple and reduce grid current THD, we use an **LCL filter**. It consists of:

- L1: inverter-side inductance
- L2: grid-side inductance
- Cf : filter capacitor (between L1 and L2)

**a. Assumptions:**

- Grid frequency: 50 Hz
- Switching frequency: 10 kHz
- Voltage per phase: 220 V (RMS)
- Peak voltage:  $V_{peak} = \sqrt{2} \times 220 = 311 \text{ V}$
- Target current ripple: 10%

**b. Output Current Estimate**

$$I_{rms} = \frac{P}{3 \cdot V_{phase}} = \frac{3000}{3 \cdot 133} \approx 7.52$$

$$I_{peak} = \sqrt{2} \cdot I_{rms} \approx 10.63$$

$$\Delta I = 0.1 \cdot I_{peak} \approx 1.063$$

**c. Inverter-Side Inductance**

$$L_1 = \frac{V_{dc}}{4 \cdot f_{sw} \cdot \Delta I} = \frac{800}{4 \cdot 10,000 \cdot 1.063} \approx 1.88 \text{ mH}$$

**d. Grid Side Inductance**

$$L_2 = 0.5 \cdot L_1 = 1 \text{ mH}$$

**e. Filter Capacitance**

$$C_f = \frac{1}{10 \cdot 2\pi f_{grid} \cdot (L_1 + L_2)} = \frac{1}{10 \cdot 2\pi \cdot 50 \cdot 3 \times 10^{-3}} \approx 106 \text{ F}$$


**f. Controller PI Tuning**

$$K_p = 2\pi f_{bp} \cdot L = 2\pi \cdot 1000 \cdot 0.002 = 12.57$$

$$K_i = 2\pi f_{bi} \cdot K_p = 2\pi \cdot 100 \cdot 12.57 = 789.6$$

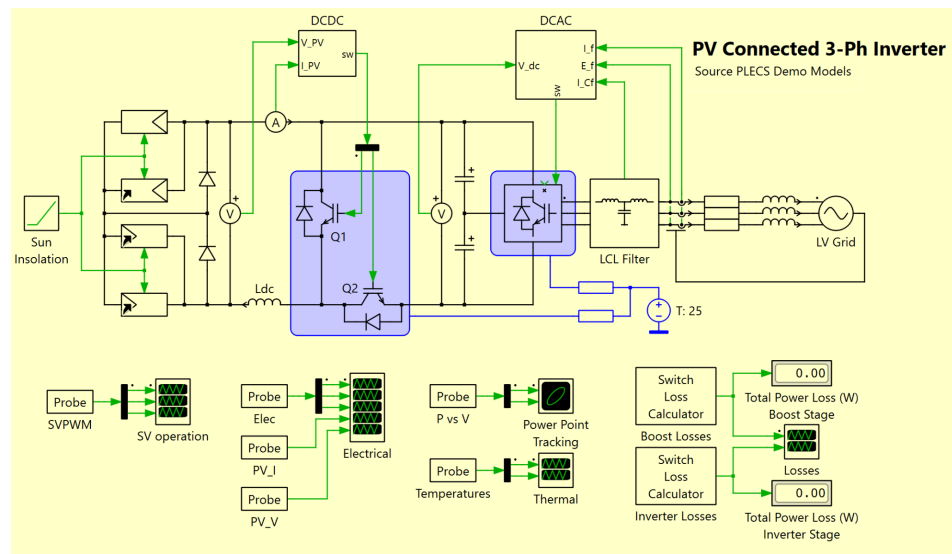
5. **Design a control system** capable of regulating both active and reactive power.

- Present your control design using block diagrams.
- Explain the method used to determine controller gain parameters.





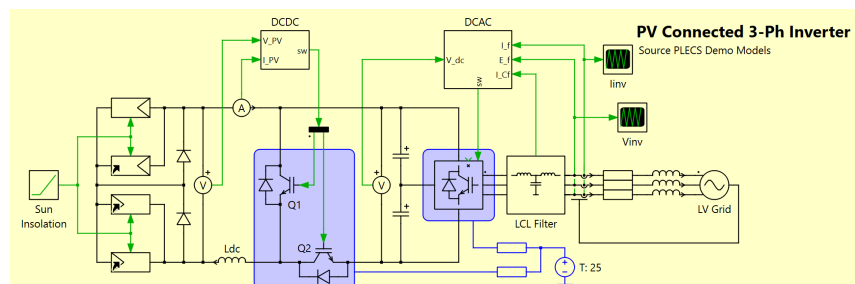
6. **Simulate and plot inverter currents** in the dq-reference frame.

- Compare reference and measured currents
- Demonstrate three operating conditions:






– In-phase current (unity power factor)

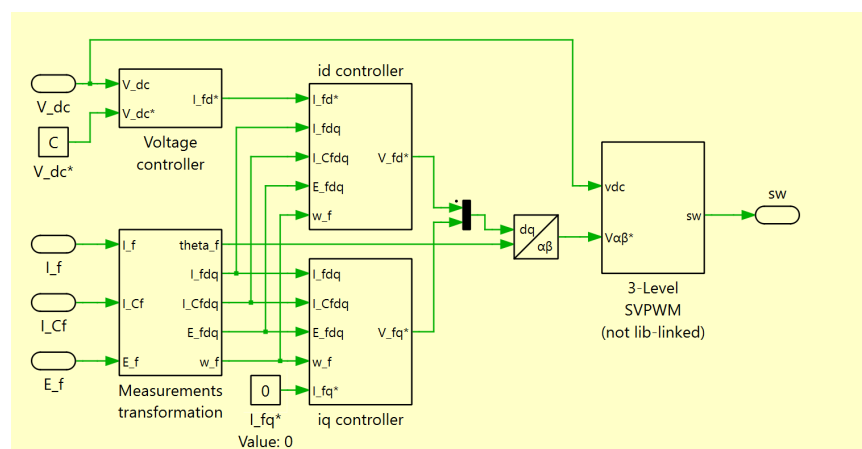

 
 



– Lagging current

 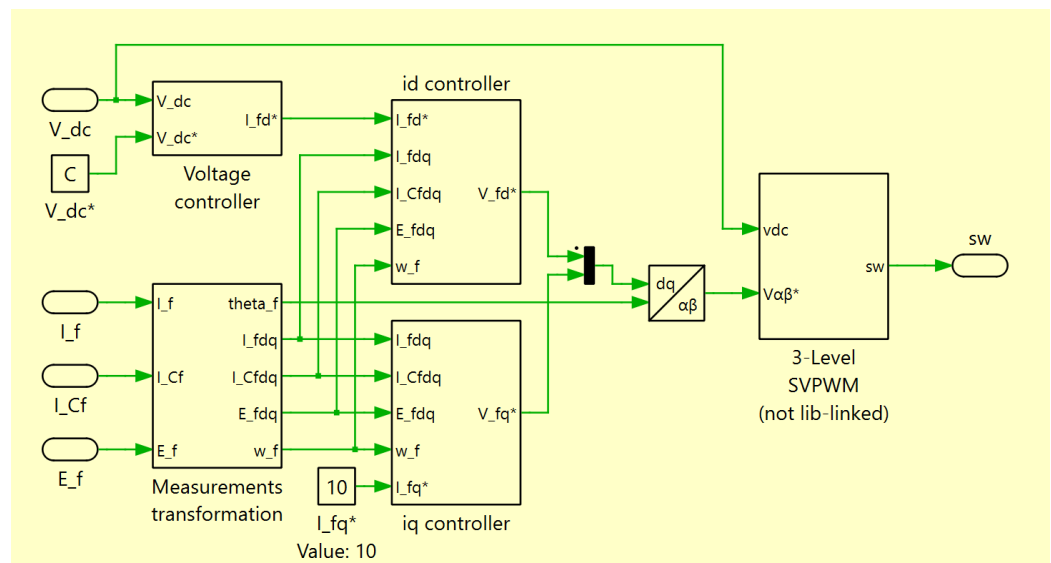

 



– Leading current

 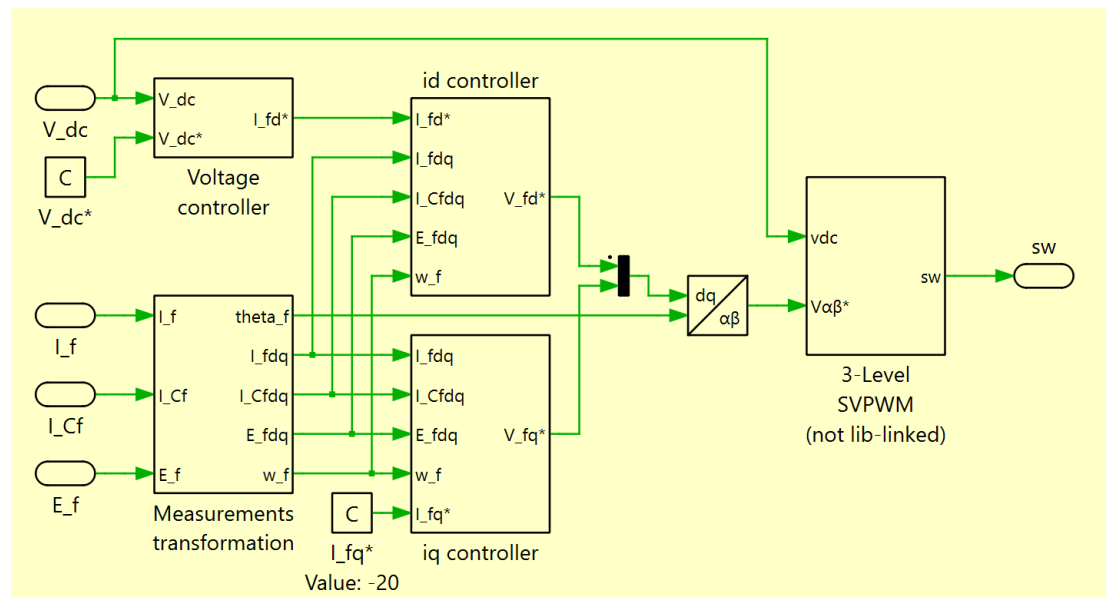


 

 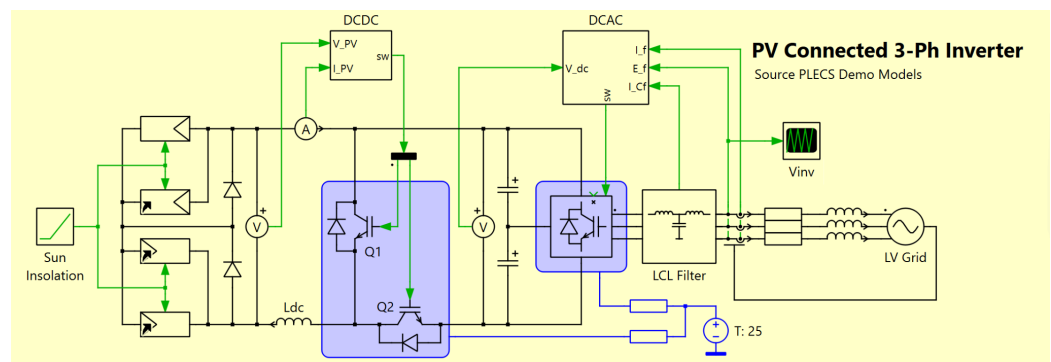7. **Plot the inverter output voltage (phase and line) in both time domain and frequency domain.**

- Perform FFT analysis on the time-domain waveform to evaluate harmonic content.



 

8. Analyze the system behavior under overmodulation conditions.
  - Show the effect of overmodulation on waveform distortion and control performance.
  - Support your analysis with simulation results.